

# Digital Logic Design

## (EL-1005)

### LABORATORY MANUAL

### Spring 2022



## LAB 01

### Introduction to Logic-Works 5

Instructor: Engr. Usama Bin Umar

Sohaib Sarosh Shamsi

---

STUDENT NAME

21K-3278

---

ROLL NO

D

---

SEC

---

FACULTY'S SIGNATURE & DATE


**MARKS AWARDED: /02**

---

NATIONAL UNIVERSITY OF COMPUTER AND EMERGING SCIENCES (FAST-NUCES), KARACHI

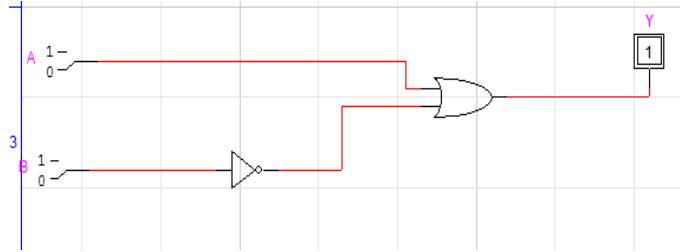**Lab #1 Tasks****Exercise # 01**


Fill up the Truth Table given below for this circuit and design it in Logic Works.



Input (A)	Input (B)	Output (Y)
0	0	1
0	1	0
1	0	1
1	1	1

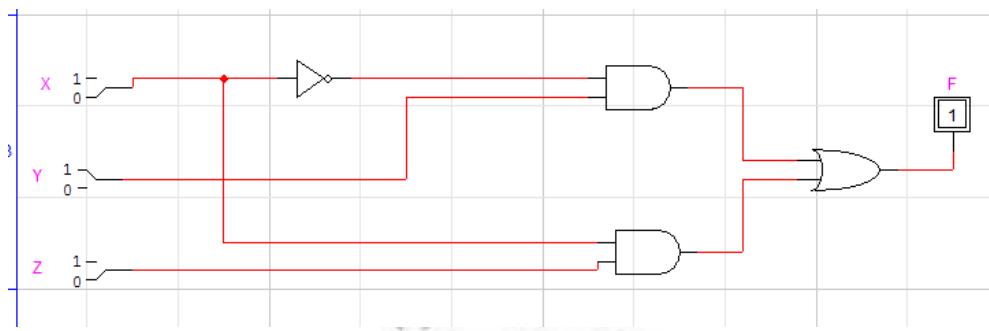**Exercise # 02**


Fill up the Truth Table given below for this circuit and design it in Logic Works



Input (X)	Input (Y)	Input (Z)	Output (F)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

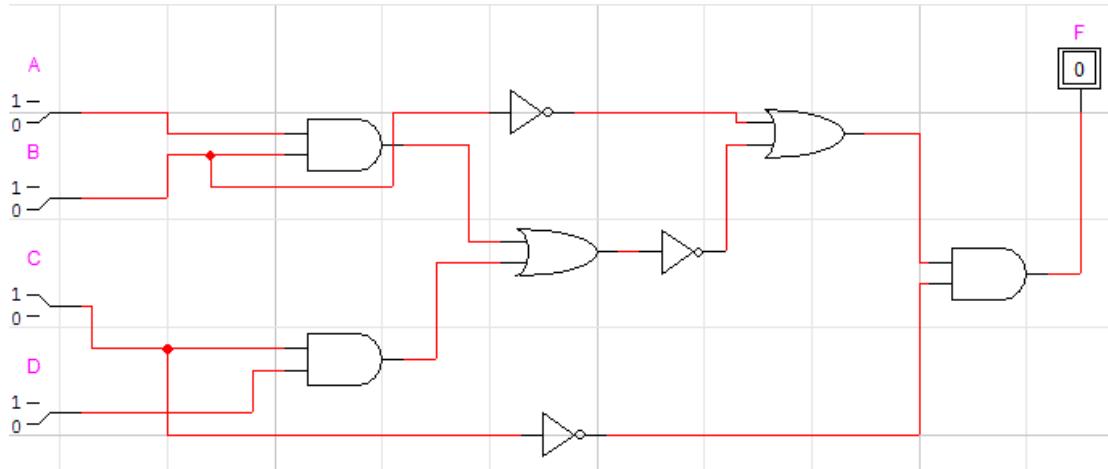**Exercise # 03**

Fill up the Truth Table given below for this circuit having four inputs.




A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0
1	1	1	1	0

## Exercise # 4


Draw the circuit diagrams for each of the Boolean expressions given below on Logic Works tool and verify the results with the help of Truth Table.

$$1. F = A + A'B$$

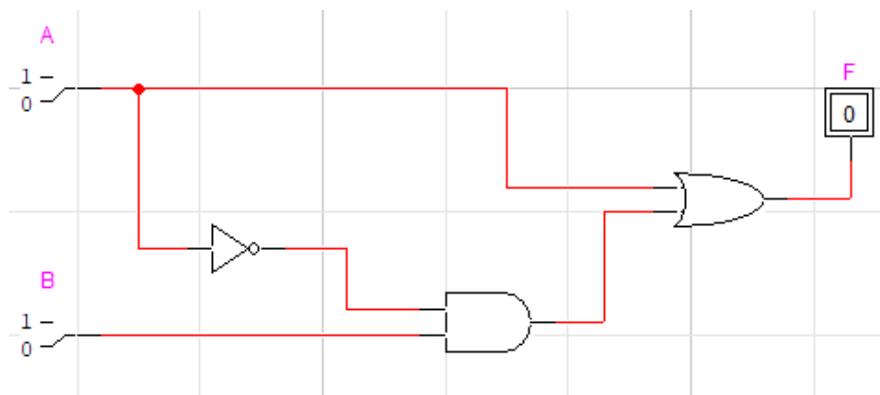


A	B	F
0	0	0
0	1	1
1	0	1
1	1	1


$$2. F = (A + B)(A + C)$$

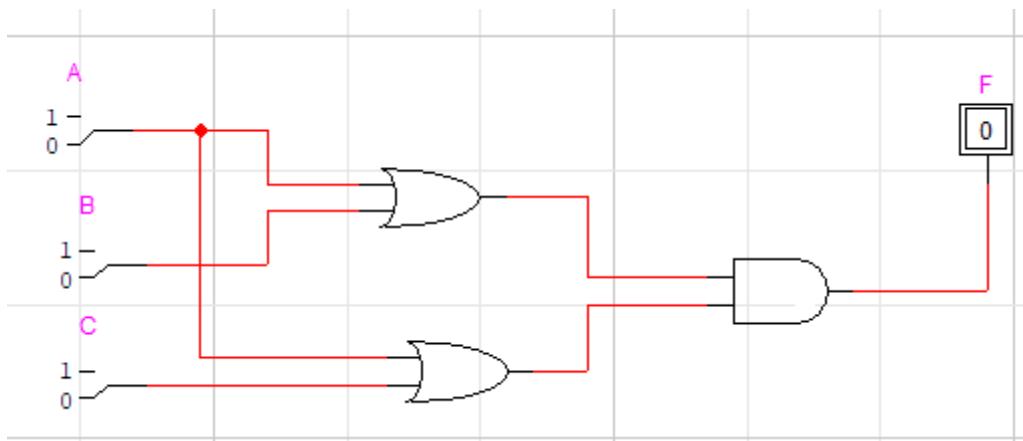

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

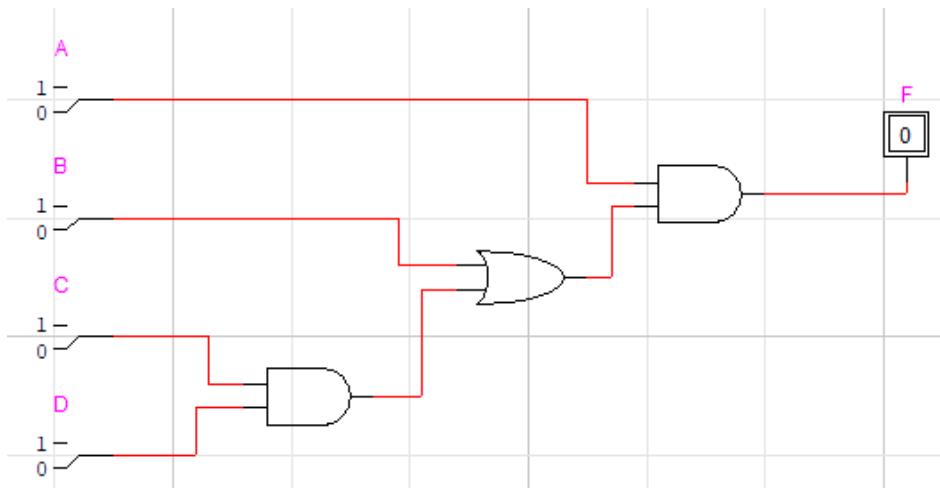
**3.  $F = A(B + CD)$** 

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

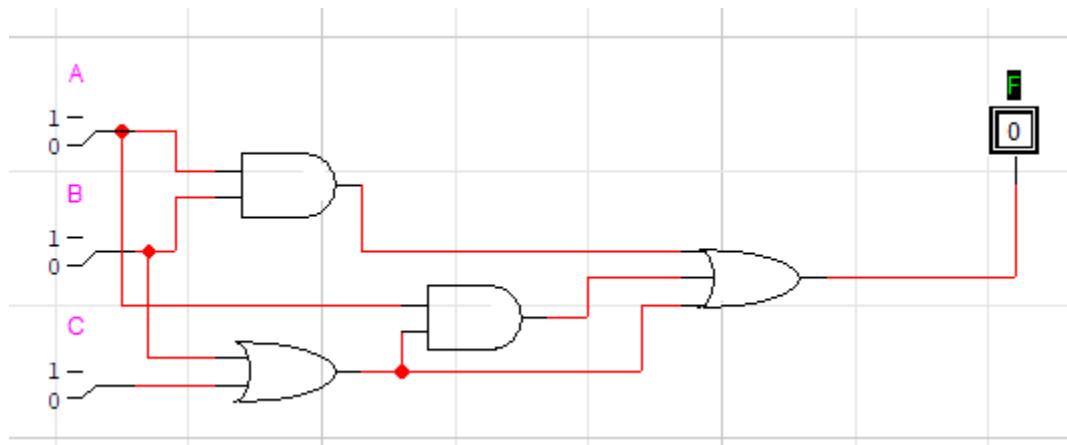
4.  $F = AB + A(B + C) + (B + C)$ 

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$5. F = X(YZ) + X'Y + (XY)Z'$$

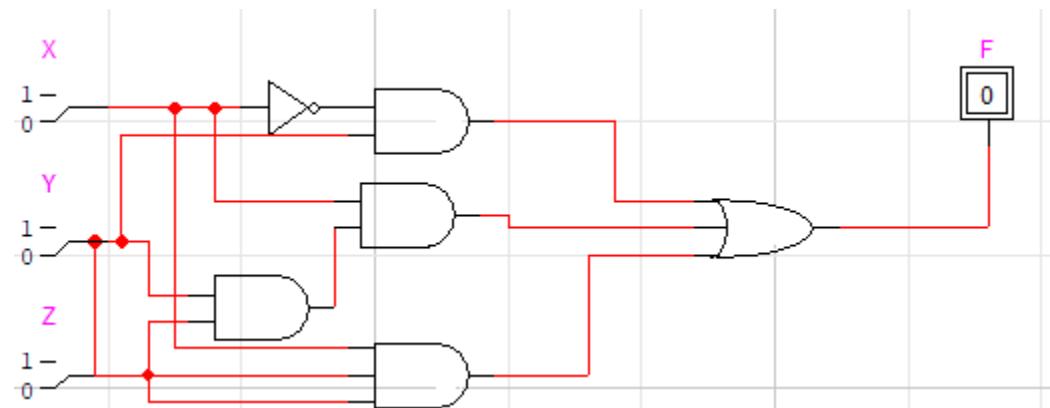

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

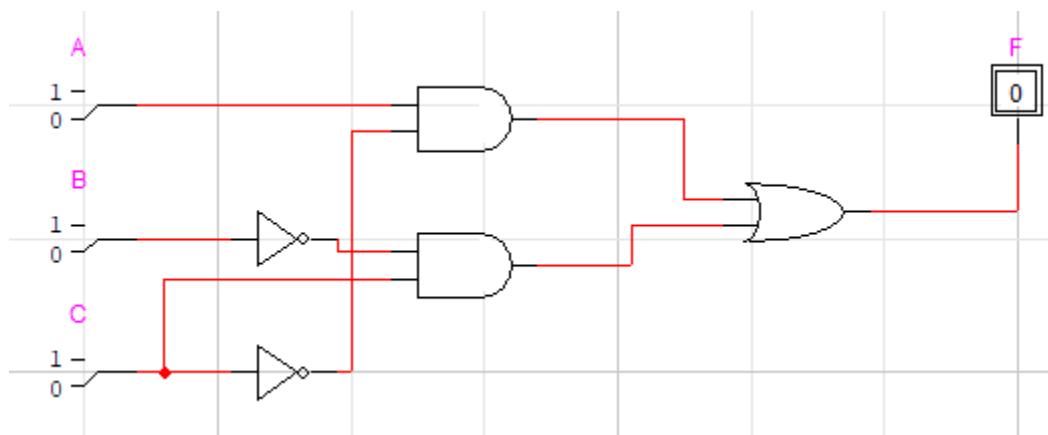**6.  $F = B'C + AC'$** 

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

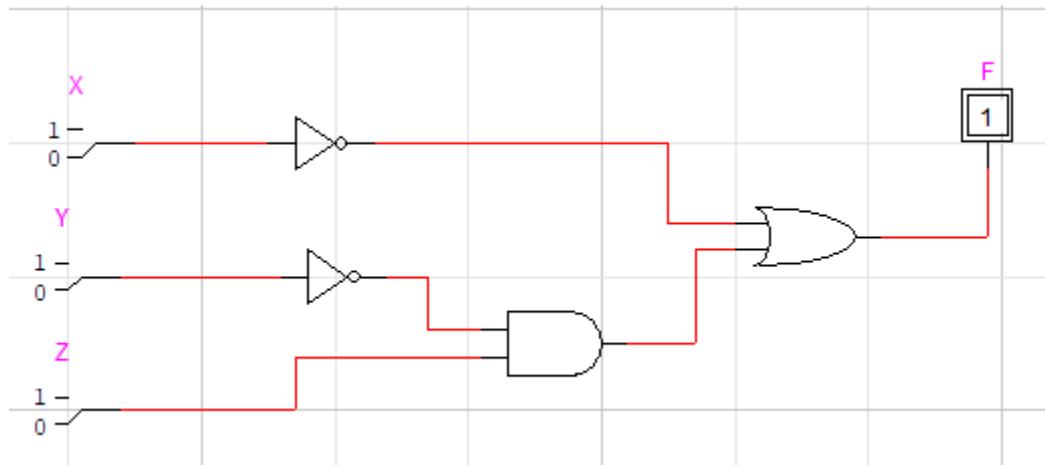**7.  $F = X' + Y'Z$** 

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0